

RTL_EXERCISE_1 BOUND FLASHER

Student: Lê Văn Tuấn Kiệt

ID: 2110300

| | |
|---------|------------|
| Author | |
| Date | 2017/03/28 |
| Version | 1.1 |

Contents

| | |
|------------------------------------|---|
| 1. Interface | 2 |
| 2. Functional implementation. | 3 |
| 3. Internal implementation. | 5 |
| 3.1. Overall. | 5 |
| 3.2. State Machine..... | 6 |
| 4. History | 6 |

1. Interface

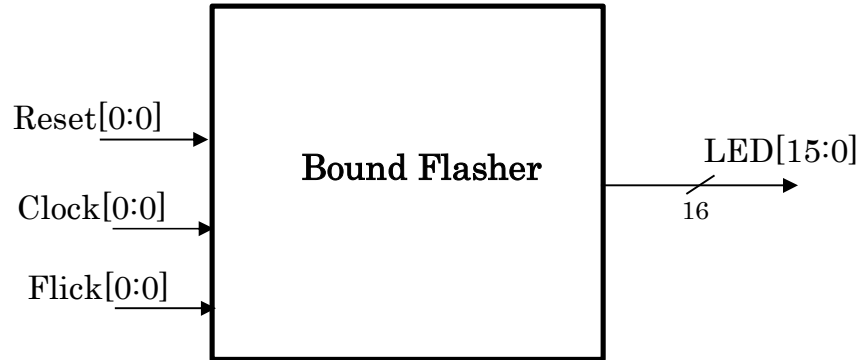


Figure 1: the figure of Bound Flasher System

| Signal | Width | In/Out | Description |
|--------|-------|--------|--------------------------------------------------|
| Reset | 1 | In | Low-active synchronous reset signal |
| Clock | 1 | In | Clock provided by system |
| Flick | 1 | In | Special input for controlling the state transfer |
| LED | 16 | Out | System LEDs |


Table 1: Description of signals in Bound Flasher

2. Functional implementation.


- Implement a 16-bits LEDs system
- System's Operation base on three input signal
 - Reset
 - Clock
 - Flick
- The system specification
 - Clock signal is provided for system inspire of function status. The function operate state's transition at positive edge of the clock signal.
 - Reset signal:
 - LOW-ACTIVE Reset = 0: System is restarted to Initial State.
 - HIGH-ACTIVE Reset = 1: System is started with initial state.
- Flick signal: special input for controlling state transfer.
- At the initial state, all lamps are OFF. If flick signal is ACTIVE, the flasher start operating:
 - The lamps are turned ON gradually from LEDs [0] to LEDs [15].
 - The LEDSs are turned OFF gradually from LEDs [15] to LEDs [5].
 - The LEDSs are turned ON gradually from LEDs [5] to LEDs [10].
 - The LEDSs are turned OFF gradually from LEDs [10] to LEDs [0].
 - The LEDSs are turned ON gradually from LEDs [0] to LEDs [5].
 - Finally, the LEDs s are turned OFF gradually from LEDSS [5] to LEDSS [0], return to initial state.
- Additional condition: At each kickback point (LEDs [5] and LEDs [0]), if flick signal is ACTIVE, the LEDs will go back and repeat that STATE. For simple, kickback point is considered only when the LEDs s are turned OFF gradually, except final state.

RTL_Exercise1 Bound Flasher

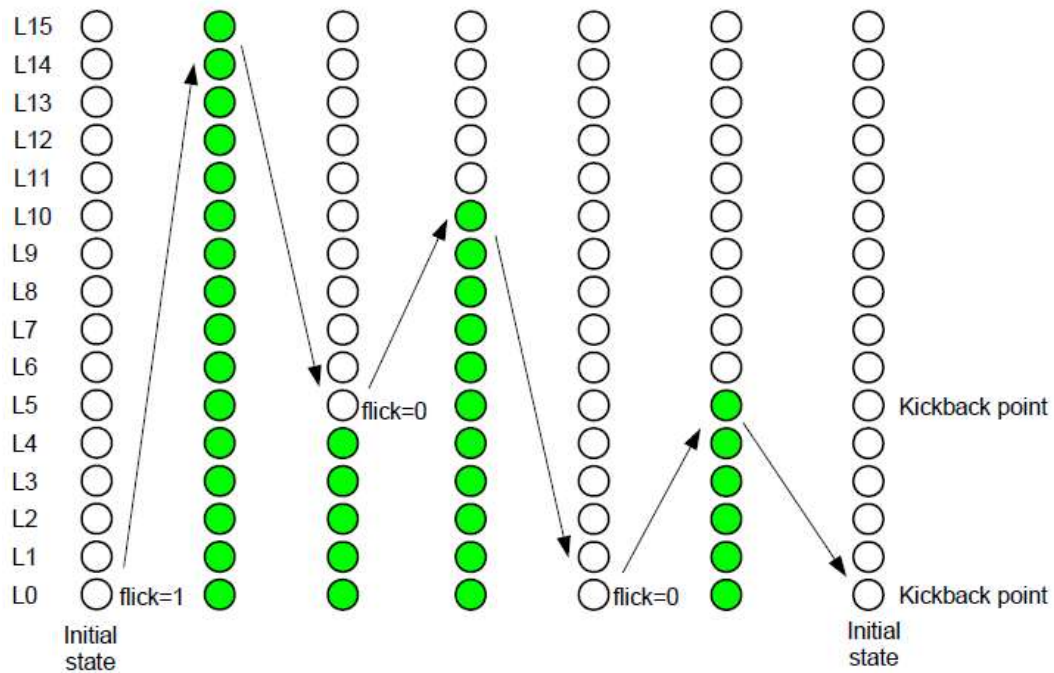- Some insulations:
 - When flick = 0 at kickback points



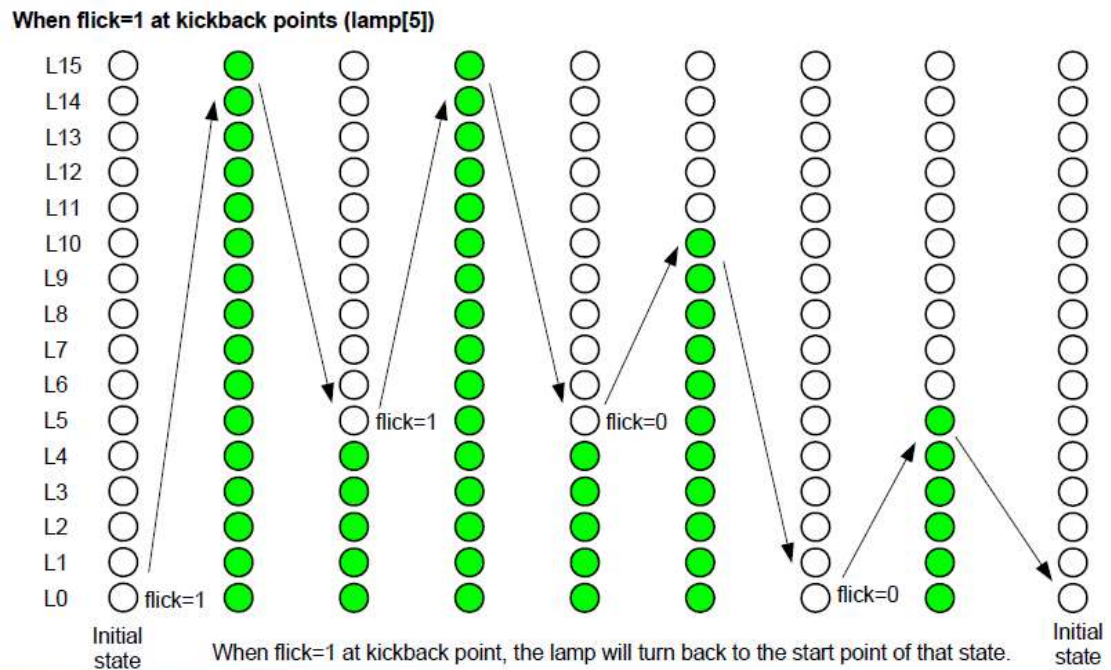- When flick = 1 at kickback points (lamp[5])



3. Internal implementation.

3.1. Overall.

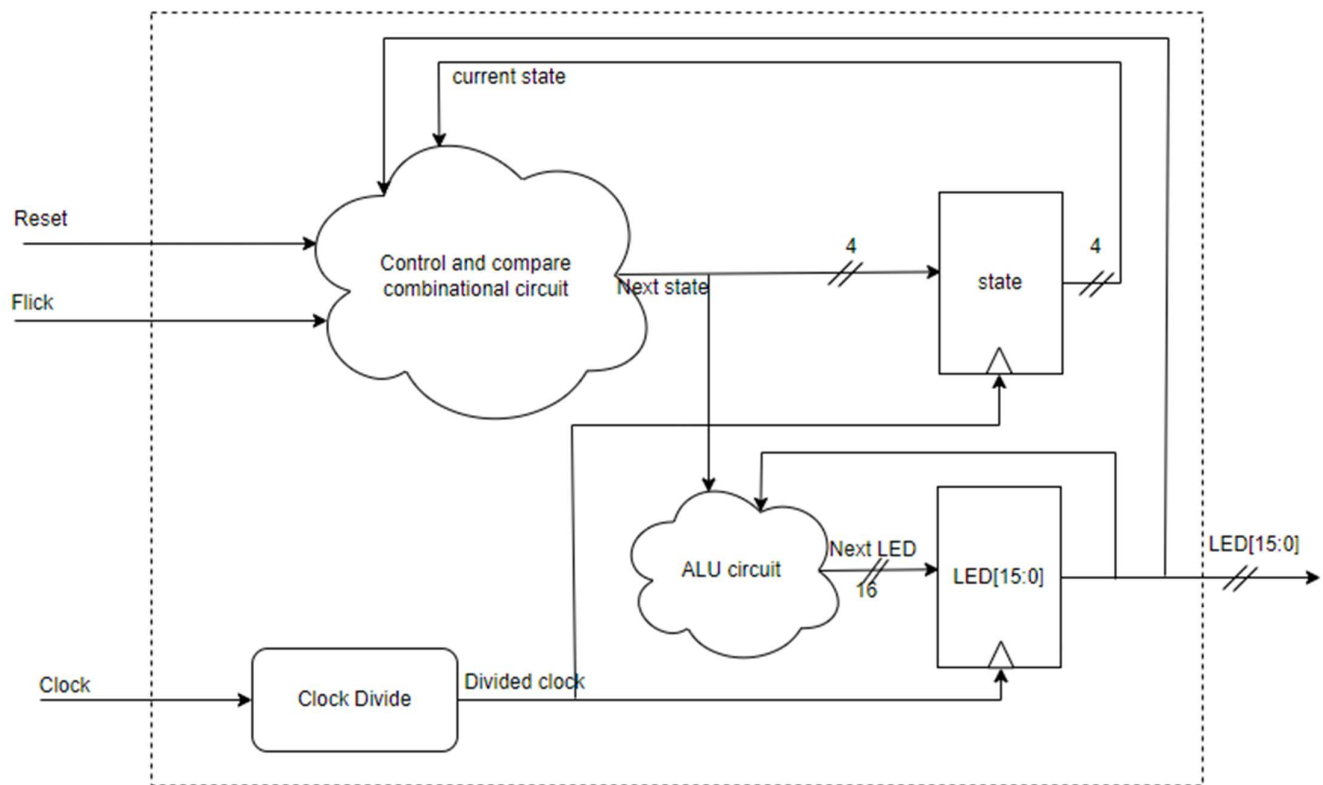


Figure 3.1: Block diagram of Bound Flasher

| Block Name | Description |
|-------------------------------------------|---------------------------------------------------------------------------------------------------------------------|
| Control and compare combinational circuit | The combinational circuit that determines next state and next value of LEDs based on current state, flick and reset |
| State | Holds state of the circuit |
| LED | The system LEDs |
| ALU circuit | The arithmetic circuit that evaluate the next value of LEDs of the next state |
| Clock divide | A circuit that creates lower frequency clock |

Table 3.1: Block diagram of Bound Flasher Description

3.2. State Machine

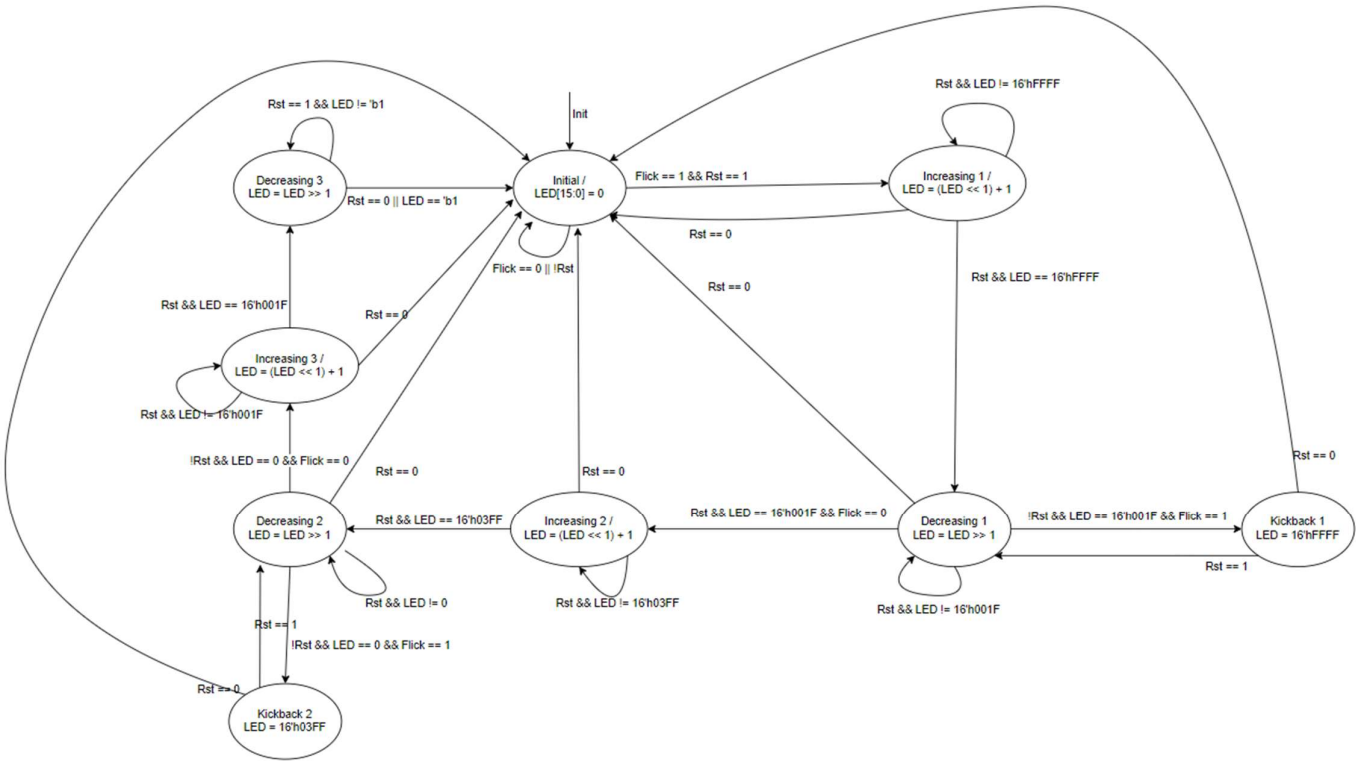


Figure 3.2: State Machine of Bound Flasher

| Variable Name | Description |
|---------------|--------------------------|
| Rst | 1-bit input Reset signal |
| Flick | 1-bit input Flick signal |
| LED | 16-bit LEDs system |

Table 3.2: variable name of State machine

| State Name | Description |
|--------------|-----------------------------------------------------------|
| Initial | Initial state in which all LEDs are turned off |
| Increasing 1 | State in which LEDs are turned on from LED[0] to LED[15] |
| Decreasing 1 | State in which LEDs are turned off from LED[15] to LED[5] |

RTL_Exercise1 Bound Flasher

| | |
|--------------|----------------------------------------------------------------------------------------------|
| Kickback 1 | Kickback point where Flick is asserted and all LEDs are turned on |
| Increasing 2 | State in which LEDs are turned on from LED[5] to LED[10] |
| Decreasing 2 | State in which LEDs are turned off from LED[10] to LED[0] |
| Kickback 2 | Kickback point where Flick is asserted and LEDs are turned on from LED[0] to LED[10] |
| Increasing 3 | State in which LEDs are turned on from LED[0] to LED[5] |
| Decreasing 3 | State in which LEDs are turned off from LED[5] to LED[0] and then return to Initial state |

Table 3.3: state name of State machine

4. History

| Date | Author | Modified part | Description |
|------------|--------|---------------|--------------|
| 2017/03/28 | | All | New creation |
| | | | |
| | | | |
| | | | |